

# E.E. 451.3/ENEL 489

## VLSI/Integrated Circuit Design

### 1998 Mid-Term Solutions

#### QUESTION #1

MARKS: 15 (3 + 3 + 3 + 3 + 3)

THE POLYSILICON LAYER IS USUALLY USED AS A SIGNAL ROUTING LAYER.  
a) GIVE 3 REASONS FOR THIS

- Has relatively low resistance.
- Has relatively low capacitance.
- Is not metal (prevents metal limited designs).
- Signals must be on polysilicon to activate a transistor. Can save a contact cut by keeping signal on polysilicon.

b)

- (IF ANY)
- None. (EXPLAIN THE DIFFERENCE BETWEEN THE TERMS FIELD, FOX + THICK OXIDE)
  - None. Realizing  $t_{ox}$  is actually the thickness. (I.e. DEVICE WELL,  $t_{ox}$  + THIN OXIDE)
  - See previous answers. Field is related to thick-oxide and device well is related to thin-oxide. Diffusion is another name for device well. (I.e. FIELD, DEVICE WELL + DIFFUSION)

See page 118 (etc) in 2<sup>nd</sup> Edition, page 68 (etc) in 1<sup>st</sup> Edition, and pages C2, C6 and Figure C.1(e) in Appendix C handout.

c) WHERE IS CANADIAN MICROELECTRONICS CORPORATION (CMC) LOCATED? (GIVE 2 COMPANIES (SIC) OR COMPANY. TECHNICAL STAFF DO NOT FABRICATE FOR CMC.)  
CMC, Room 210A, Carruthers Hall, Queen's University, Kingston, Ontario, K7L 3N6

Nortel	BiCMOS, CMOS5, FT25 (CMOS3DLM is no longer used)
Mitel	Mitel15
Gennum	GA911
MOSIS	CMOSIS5
Vitesse	GaAs

"So, I want you to get up now.  
I want all of you to get up out  
of your chairs. I want you to  
get up right now and go to the  
window, open it, and stick your  
head out and yell, 'I'm mad as  
hell and I'm not going to take  
this anymore!'"

March 4, 1998

E.E. 4

N-channel transistors  
transistors are character

i)

For n-channel transistors,  
cut-off mode (i.e., off). G  
transistor connected to  $V_{ss}$   
(e.g., 4.3V).

Similarly for p-channel transistors, the typical  $V_t$  is on the order of  $-0.7V$ . Given the minimum gate voltage would be  $V_{ss}$  and one side of the transistor connected to  $V_{ss}$ , the smallest voltage which could be passed would be  $(V_{ss} - V_t)$  (e.g.,  $+0.7V$ ).

See pages 86-87 in text for similar explanation.

e) LIST 3 Modes of operation of a MOS transistor & briefly describe each one.

- Cut-off. When  $V_{gs} < V_t$ , the transistor is effectively turned "off" (there is still a small
- Linear. When  $V_{gs} \geq V_t$  and  $V_{ds} < (V_{gs} - V_t)$ , the current flow is approximately proportional to  $V_{ds}$ .
- Saturation. When  $V_{gs} \geq V_t$  and  $V_{ds} > (V_{gs} - V_t)$ , the current flow is approximately a constant independent of  $V_{ds}$ .

Question confused some as should have asked for three "regions" as opposed to modes. Many mixed regions with modes (inversion, accumulation, etc.). So marks were given for either/or.

f) Why does Metal1-Field has a capacitive edge component but not Metal1-polysilicon or Metal1-diffusion?  
The field (substate in this case) can be thought of as a large plane relative to the metal1 lines. Therefore you get fringing effects from the perimeter of metal1 to the field "plane". Polysilicon and diffusion are usually relatively small areas on the die and therefore do not act like planes relative to metal1 and thus the fringing effects can usually be ignored.



Exam File Provided By  
The UofS IEEE Student Branch

ieee.usask.ca

Student Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

## QUESTION #2

MARKS: 15 (5 + 5 + 5)

- Consider the pseudo-MOS inverter shown below. Given  $V_{in} = 5V$  & the max. d) target  $V_{out} = 0.2V$ , what is minimum value of resistor  $R$ ? It is made of polysilicon, what is the physical size of resistor  $R$ ? Is this a realistic size to implement on an IC?
- Given  $V_{out} = V_{ds} = 0.2V$  realistic size to implement on an IC?
- $V_{in} = V_{gs} = 5V$
- $V_t = 0.7V$  (for an n-channel CMOS3DLM)

Therefore, since  $V_{gs} > V_t$  and  $V_{ds} < (V_{gs} - V_t)$ , the transistor is in "linear" mode.

The current flow through a transistor in linear mode is given by:

$$I_{ds} = \beta[(V_{gs} - V_t)V_{ds} - V_{ds}^2/2]$$

$$\beta = \mu \frac{\epsilon_{ox}}{t_{ox}} \left( \frac{W}{L} \right)$$

Since the same current that is flowing through the transistor is flowing through the resistor:

$$V_{ds} = I_{ds} \times R + 0.2V$$

$$R = \frac{4.8V}{(755 \text{ cm}^2 / \text{V sec}) \frac{3.9 \times 8.854 \times 10^{-14} \text{ F/cm}}{5 \times 10^{-6} \text{ cm}} [4.3 \times 0.2 - 0.2^2 / 2]}$$


$$R = 106.8 \text{ k}\Omega$$

For polysilicon, resistance =  $18\Omega/\text{square}$

$$\text{Length in squares} = \frac{106.8 \text{ k}\Omega}{18\Omega/\text{square}} = 5933$$

Since minimum poly width =  $3\mu\text{m}$ , length =  $17,800\mu\text{m}$  (17.8mm)

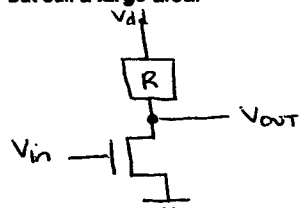The length is longer than most chips so this is NOT realistic! Could be done as a serpentine but still a large area.



Student Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

Consider a Minimum Sized inverter (MSI) to be the smallest inverter possible w/ equal rise & fall times.


- i) For CMOS3DLM,  $\mu_n = 775 \text{ cm}^2 / \text{Vs}$   
 $\mu_p = 250 \text{ cm}^2 / \text{Vs}$

ii) What are the sizes of the n-channel & p-channel transistors in such an MSI?

Therefore, n-channel:  $3\mu\text{m}$  wide by  $3\mu\text{m}$  long

$$\text{p-channel: } \frac{775}{250} \times 3 = 9.3\mu\text{m wide by } 3\mu\text{m long}$$

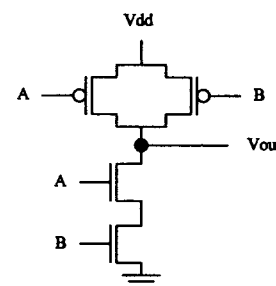- ii) Consider the diagram for a NAND gate:



For  $V_{out} = 1$ , one p-channel transistor will be "pull up" (worst case scenario). Thus the p-channel should be the same size as for the MSI.

For  $V_{out} = 0$ , two n-channel transistors are in series. Thus they must each have half the resistance of the n-channel in the MSI, therefore they must be twice as wide.

n-channel:  $6\mu\text{m}$  wide by  $3\mu\text{m}$  long

p-channel:  $9.3\mu\text{m}$  wide by  $3\mu\text{m}$  long

- iii) Consider the gate capacitance seen on the input of the two types of gates. The gate capacitance is proportional to the gate area:

$$\text{For MSI, gate area} = 3 \times 3 + 9.3 \times 3 = 36.9 \mu\text{m}^2$$

$$\text{For NAND, gate area} = 6 \times 3 + 9.3 \times 3 = 45.9 \mu\text{m}^2$$

Thus the relative speed of driving a NAND versus driving an MSI =  $36.9 / 45.9 = 80\%$

ii) What are the required sizing of the transistor in a 2-input NAND gate which drives an MSI so that it has the same worst case delays as an MSI driving an MSI?

iii) How much slower will the above 2-input NAND gate be driving an identical 2-input NAND gate compared to driving an MSI?


Student Name: \_\_\_\_\_

Student Number: \_\_\_\_\_


c)

No, the circuit does not function as intended. D is driving against  $\bar{Q}$ , Q follows  $\bar{D}$ , and the output from the "first stage" (indicated by "X") does not go anywhere!

The correct circuit should be:

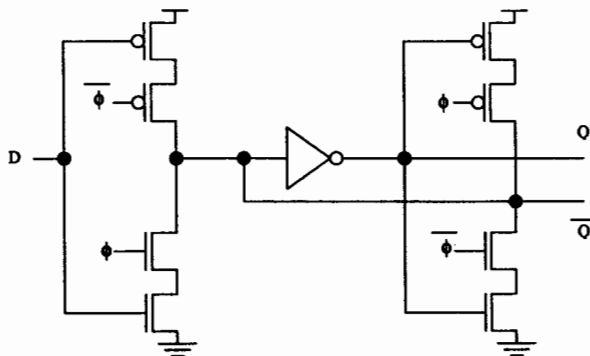

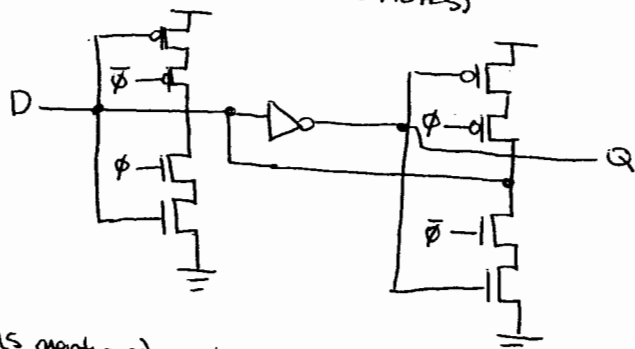\* Consider the diagram below: design domain abstraction of a D-type static latch. THE circuit is shown (as previously in class notes)



As mentioned in class, sometimes the design domain abstraction loses track of what the designer intended (reality). Does the circuit function as intended? If not, clearly show your connected circuit.

Student Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

## QUESTION #3

MARKS: 15 (10 + 5)

Some things to consider:

- Circuit is not correct. I am assuming you are using the correct circuit.
- A STICKS diagram is done using lines, NOT polygons, rectangles, etc. Do NOT show physical layout since this would take way too long.
- Inputs on metal must get to polysilicon. Therefore 3 contact cuts.
- With outputs on metal may need as many as 4 contact cuts.
- Phi and PhiBar need at least 2 contact cuts to swap sides (top to bottom). Maybe as many as 4.
- Each transistor pair (i.e., in an inverter) contains 5 contact cuts. This assumes output is on polysilicon.
- Each transistor set (2 n-channel and 2 p-channel, i.e., in a clocked inverter) contains 5 (NOT 9) contact cuts. This assumes output is on polysilicon.
- With two substrate contact of each type there is about 24-30 contact cuts. We may be able to do it with less (if things work out) but it is unlikely.
- A single transistor is about 25 dsm high and about 15 dsm wide. The width can be reduced by "hiding" the polysilicon overlap of diffusion but will still be 9 dsm wide (due to contact cut on source and drain). Rules A.2, A.3, A.6, A.7, C.5, D.7, and Rules A.2, A.6, C.5, and E.1.
- A series combination of two transistors is about 35 dsm high and about 15 dsm wide. The width can be reduced by "hiding" the polysilicon overlap of diffusion but will still be 9 dsm wide (due to contact cut on source and drain). Rules (see above) and B.3.
- $V_{DD}$  and  $V_{SS}$  lines are 9dsm wide (due to the contact cuts in them). Rules A.6, C.5.
- Don't forget that p+ diffusion and P-well must be spaced 14 dsm apart. Rule D.1.
- There are two choices for STICKS diagram organization. Vertical transistors and Horizontal transistors. A STICK solution is shown for each. Note that I have left the "white-space" in these diagrams to make them easier to read. If I was to do a physical layout I would concentrate on these spots in order to optimize the size.
- Note that the  $\phi$  and  $\bar{\phi}$  signal go from bottom to top and vice versa. If the cells had to be stacked end-to-end, this would allowed the cascading to be done efficiently by automatically making the right connections.

Q draw Sticks diagram for D-type static latch from 2 (c). correct circuit if needed.


1. Inputs must come in from left (Met.1)
2. Outputs must exit from right (Met.1)
3. Analysis both clock phases ( $\phi$  &  $\bar{\phi}$ ) are generated externally
4. No connection wires are allowed outside  $V_{DD}$  &  $V_{SS}$  power rails.
5.  $V_{DD}$  power rail should be at the top &  $V_{SS}$  at the bottom.
6. At least 2 substrate connections (of each type) shown
7. No Met. 2 allowed
8. Standard Sticks colors for CMOS 3P1M to be used.

Student Name: \_\_\_\_\_


Student Number: \_\_\_\_\_

- good CMOS circuit design guidelines are to be used.

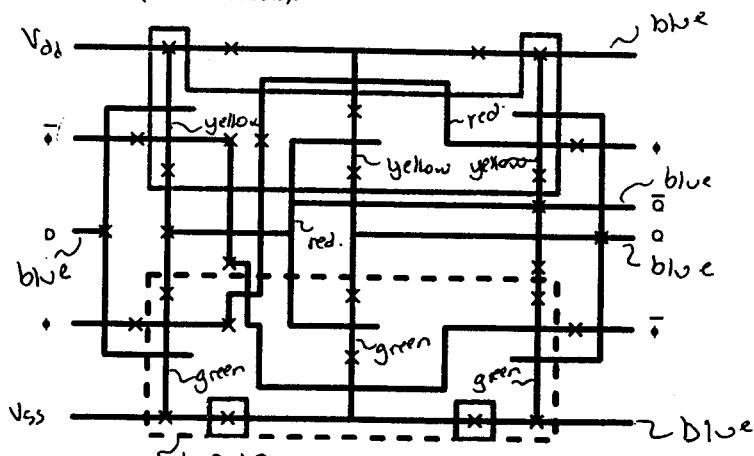Vertical transistor version (29 contact cuts):



Horizontal version ( 29 contact cuts):

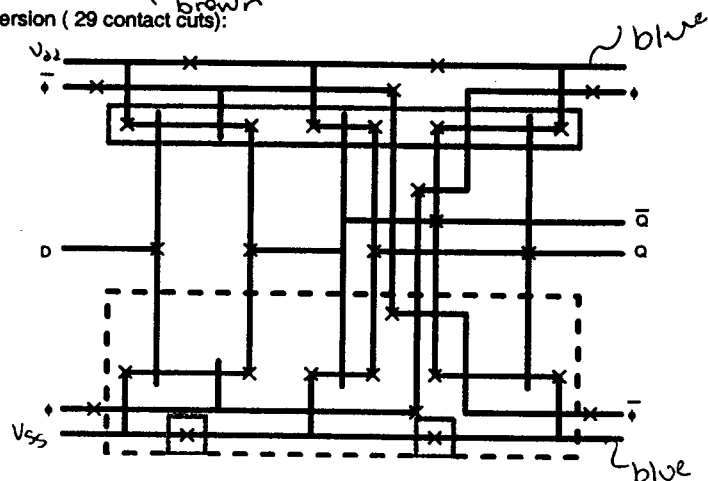

Horizontal transistors:  $9 + 5 + 9 + 14 + 9 + 5 + 9 = 60 \text{ dsm}$   
Vertical transistors (worst case):  $9 + 35 + 14 + 35 + 9 = 102 \text{ dsm}$

Note that some assumptions have been made about "hiding" some of the connections.

Estimate height, in <sup>design scale</sup> microns, of a physical layout based on D-type sticks diagram. Height is defined as the distance from top led to bottom vs. Do not do a detailed calculation.

Student Name: \_\_\_\_\_ Student Number: \_\_\_\_\_

[Students] "I don't understand enough of this to formulate